

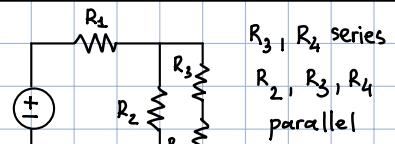


Power: work / unit of time  
Power across component:  
 $P = v \cdot i$

Ohm's Law: applies to a resistor

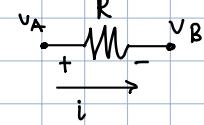


Resistors in series:

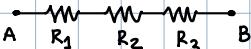


$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_N$$

Resistors in parallel:
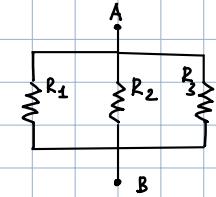
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$




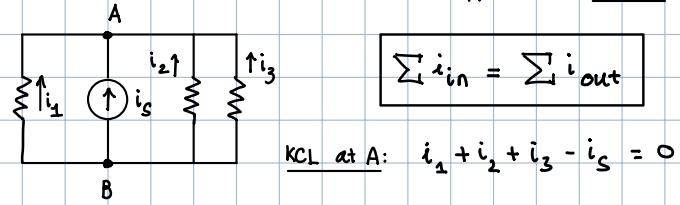Kirchhoff's Current Law (KCL): Applies to nodes




$$\text{KCL at A: } i_1 + i_2 + i_3 - i_S = 0$$

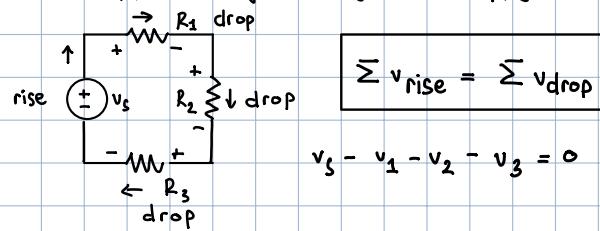Kirchhoff's Voltage Law (KVL): Apply to mesh



$$\sum v_{rise} = \sum v_{drop}$$


Voltage division: Series only

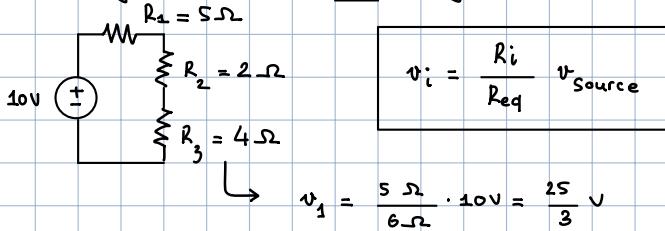

$$v_i = \frac{R_i}{R_{eq}} v_{source}$$

$$v_1 = \frac{5 \Omega}{6 \Omega} \cdot 10V = \frac{25}{3} V$$

Current division: Parallel only

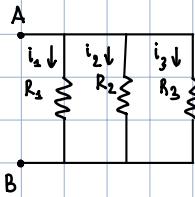


$$i_i = \frac{R_{eq}}{R_i} \cdot i_{source}$$

Nodal Voltage Method:

- Identify number of nodes and name them.
- Select ground node  $\Rightarrow$  choose one with most branches
- Identify known node voltages.
- Assume current direction  $\Rightarrow$  Apply KCL on known nodes
- Solve using Ohm's Law.

Example: Solve for voltages at each node

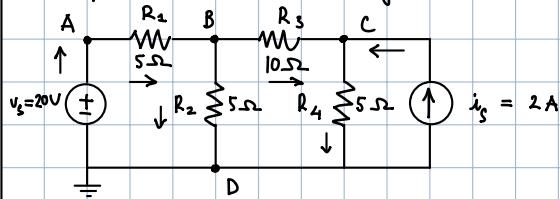

1/ Select ground node at node D.

$$\Rightarrow v_D = 0V ; v_A = 20V \text{ (20V voltage rise)}$$

2/ KCL on nodes B and C:

$$i_1 - i_2 - i_3 = 0 \quad (1) ; \quad i_3 + i_4 - i_4 = 0 \quad (2)$$

$$i_1 = \frac{v_1}{R_1} = \frac{v_A - v_B}{5\Omega} = \frac{20 - v_B}{5} ; \quad i_2 = \frac{v_2}{R_2} = \frac{v_B - v_D}{5\Omega} = \frac{v_B}{5}$$

$$i_3 = \frac{v_3}{R_3} = \frac{v_B - v_C}{10\Omega} ; \quad i_4 = \frac{v_4}{R_4} = \frac{v_C - v_D}{5\Omega} = \frac{v_C}{5}$$


Plug into (1) (2) to solve.

Mesh current method


- Identify and name meshes
- Identify known current (current part of 1 mesh)
- Assign clock-wise current flow in mesh and assign signs (+/-) to resistors following passive sign convention. (PSC)
- Solve using KVL

Current as combination of meshes:

$$i_R = i_B - i_A \text{ (PSC)}$$

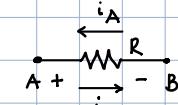


Example:

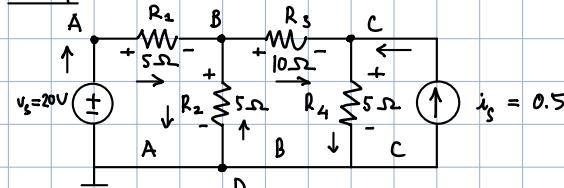


$$\text{Mesh A: } v_s - v_1 - v_2 = 0 \Rightarrow 20 - 5i_1 - 5i_{2A} = 0$$

$$\text{Mesh B: } v_{2B} - v_3 - v_{4B} = 0 \Rightarrow 5i_{2B} - 10i_3 - 5i_{4B} = 0$$

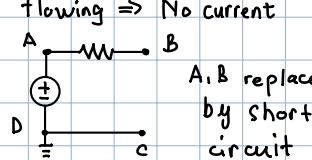Open circuit: No charge flowing  $\Rightarrow$  No current



Short circuit: Same Voltage

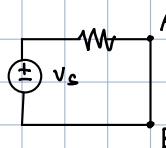


Supernode: Only exists when doing Node voltage.

Non grounded voltage source

Not know current through voltage source  $\Rightarrow$


Remove voltage source.

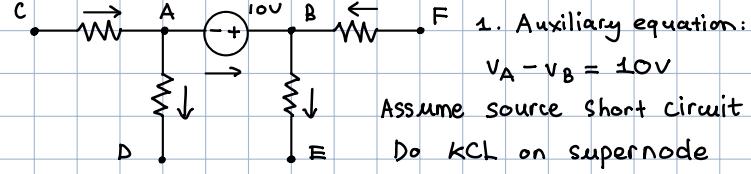

Supermesh: Current source between 2 adjacent meshes

Do Not know voltage across the current source

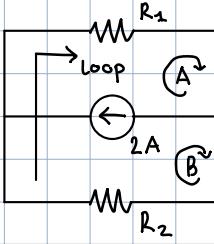Remove branch with shared current source.



$$\text{Auxiliary eq: } i_A - i_B = 2A$$


KVL on the whole supermesh

Principle of superposition:

- Calculate contribution ( $v_k$ ;  $i_k$ ) of each source  $\Rightarrow$  solve for equivalence resistance ( $R_{TH}$  or  $R_N$ )
- Turn off all sources; leave 1 on

Define  $v$  or  $i$  to be found and solve for contribution of each source:
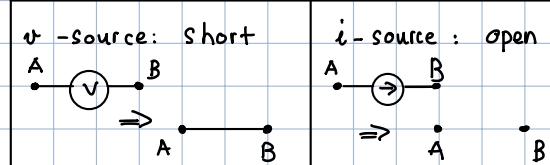
$$i_{\text{total}} = i_{v\text{-source}} + i_{i\text{-source}}$$



### THÉVENIN CIRCUIT:

• Thévenin equivalent resistance  $R_{TH}$ :


1. Remove load (open circ) and turn off all sources.
2. Solve for equivalent resistance

• Thévenin equivalent voltage:

1. Remove the load, leaving the load terminals open.
2. Define  $v_{TH}$  across the open terminals.
3. Solve for  $v_{TH}$ .

• Thévenin equivalent circuit:

Voltage source + resistors in series.

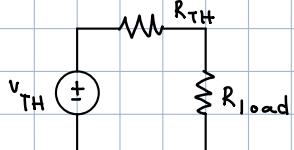

$$R_{TH} = \frac{V_{TH}}{I_N}$$

### NORTON CIRCUIT


• Norton equivalent resistance  $R_N$ :

1. Remove load (open circ) and turn off all sources.
2. Solve for equivalent resistance

• Norton equivalent current:


1. Replace load with short circuit.
2. Define the short circuit's current as Norton's equivalent current  $i_N$
3. Solve for  $i_N$

• Norton's equivalent circuit:

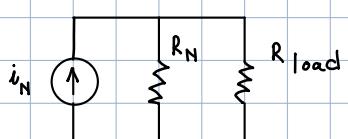


$$V_{TH} = I_N \cdot R_{TH}$$

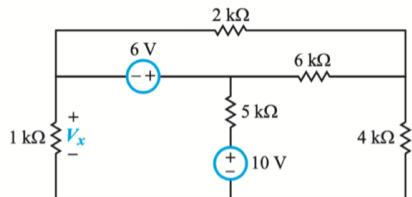Example:  $1k\Omega$  resistor is the load, find Norton and Thévenin:



Thévenin:

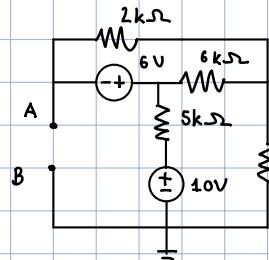

Solve using nodal voltage

Watch out for the


supernode

$$v_A = 1.381V$$

$$v_B = 0V$$

$$v_{TH} = 1.381V$$



Norton

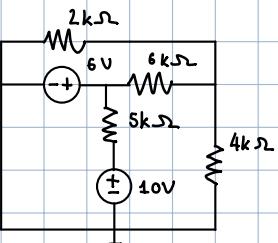

Solve using nodal voltage

$$i_N = 5.27 \times 10^{-4} A$$

1/ Find equivalent resistance:

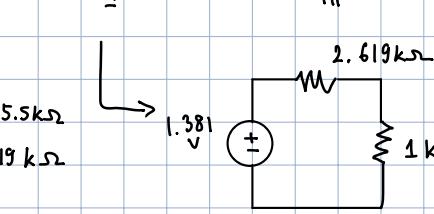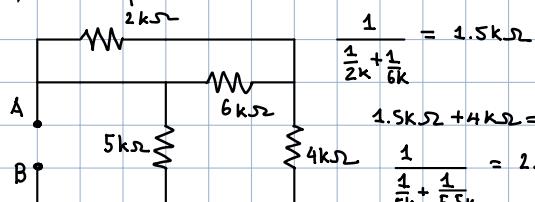

CAPACITORS: Unit: Capacitance [C]   
Stores energy between electric field between 2 plates  
PSC

$$C = Q/V$$

$$i_C = i \left( \frac{dV}{dt} \right)$$

$$v_C = \frac{1}{C} \int_0^t i_C(t) dt + v_0$$

Steady state:  
Open circuit


In parallel:  $C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$

In series:  $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$

1st Order circuit: contains 1 energy storage device : RL or RC circuit  
Time constant  $\tau$ : controls exponential rate of decay

RC circuit: Transient response

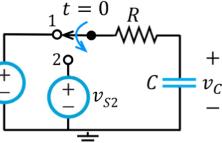1. Calculate  $v_C(0)$
2. Calculate steady State  $v_C(\infty)$
3. Solve for transient response by finding Thévenin equivalent circuit with capacitor as the load.



$$v_C(t) = v_C(\infty) + (v_C(0) - v_C(\infty)) e^{-1/R_T C} +$$

SINUSOIDAL SIGNAL: A: Amplitude ;  $\varphi$ : phase

$$v_{AC} = A \cos(\omega t + \varphi)$$

$$\omega = 2\pi f$$

$$f = \frac{1}{T}$$

w: frequency shift

$\varphi < 0$ : shift right

$\varphi >$ : shift left

T: period ; f: frequency

\* Sine to Cosine signal:

(Hz)

$$\text{Phase shift } 90^\circ \text{ to the right: } A \sin(\omega t - 90^\circ) = A \cos(\omega t)$$

PHASOR DOMAIN: transform from time domain to phasor domain to avoid sine and cos

$$v(t) = A \cos(\omega t + \varphi) \Rightarrow v(wj) = Ae^{wj}$$

Impedance: Ratio between phasor voltage and phasor current

$$Z = \frac{V}{I}$$

Resistors	$Z_R = R$
Capacitors	$Z_C = \frac{1}{j\omega C}$
Inductors	$Z_L = j\omega L$

INDUCTORS: Unit: Henry [H]   
Store energy in magnetic field in coil loop.  
PSC

$$L = \Phi_B / I$$

$$v_L = L \left( \frac{di_L}{dt} \right)$$

$$i_L = \frac{1}{L} \int_0^t v_L(t) dt + i_0$$

Steady state short circuit

In series:  $L_{eq} = L_1 + L_2 + \dots + L_N$


In parallel:  $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$

$$\tau = RC$$

$$\tau = R/L$$

RL circuit: transient response

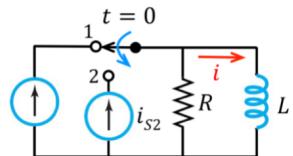1. Calculate  $i_L(0)$
2. Calculate steady  $i_L(\infty)$
3. Solve for transient response by solving Norton circuit with L as a load.



$$i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{(-R_N/L)t}$$

COMPLEX NUMBER:

Rectangular :

$$z = a + bj$$

$$\operatorname{Re}[z] = a$$

$$\operatorname{Im}[z] = b$$

Polar :

$$z = m \angle \theta = me^{\theta j}$$

$$\text{Magnitude } |z| = m$$

$$\text{Phase } \angle z = \theta$$

$$\text{Rec} \rightarrow \text{Polar} : m = \sqrt{a^2 + b^2} ; \theta = \tan^{-1}(b/a)$$

$$\text{Polar} \rightarrow \text{Rec} : a = m \cos \theta ; b = m \sin \theta$$

AC circuit Analysis:

1. Write sources in cosine form.
2. Convert to phasor domain
3. Use source frequency to write impedances for components ; redraw in phasor form.
4. Use DC circuit methods  $\Rightarrow$  convert back to time domain

Phasor domain equivalent circuit:

Find Norton and Thévenin equivalent circuits in phasor domain.

AC Power: Given:  $v(t) = v_m \cos(\omega t + \phi_v)$   
 $i(t) = i_m \cos(\omega t + \phi_I)$

$$P = \frac{1}{T_0} \int_0^{T_0} v(t)i(t) dt = \frac{V_m I_m}{2} \cos(\phi_v - \phi_I) = \frac{V_m I_m}{2} \cos(\phi_z)$$

$\Rightarrow$  Average amount of work done or energy transferred per unit time

Average Power for Components: Polar Form only!

Resistors:  $Z_R = R e^{0j} \Rightarrow P_R = \frac{V_m \cdot I_m}{2}$

Capacitor:  $P_c = 0$

Inductors:  $P_L = 0$

Ohm's Law in phasor form:

$$V = IZ$$

$$V = V_m e^{\phi_v j}$$

$$I = I_m e^{\phi_I j}$$

$$Z = \frac{V_m}{I_m} e^{(\phi_v - \phi_I)j}$$

$$Z_m = \frac{V_m}{I_m}$$

$$\phi_z = \phi_v - \phi_I$$

\*: complex conjugate

m: magnitude

$$X \cdot X^* = X_m^2$$


$$X_m \angle \theta_X \cdot X_m \angle -\theta_X$$

$$X_m^2 < 0$$

$V_{in}$  and  $I_{in}$  are independent voltage / current source;  $V_{out}$ ,  $I_{in}$  are freely chosen.

Frequency response: measure how circuit responds to sinusoidal inputs of arbitrary frequency.

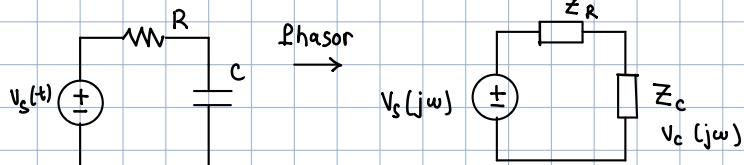
Low pass Filter: Signals with high  $\omega$  filtered out.



$$V_c(j\omega) = \frac{1}{1+j\omega CR} \cdot V_s(j\omega) \Rightarrow \text{voltage division}$$

$$H = \frac{V_c(j\omega)}{V_s(j\omega)} = \frac{1}{1+j\omega CR}$$
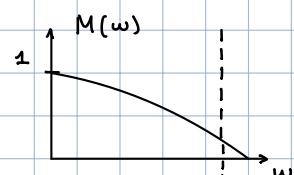
$$M(\omega) = \frac{1}{\sqrt{1 + (\omega CR)^2}}$$



As  $\omega \rightarrow 0$ ,  $M(\omega) \rightarrow 1$

$\omega \rightarrow \infty$ ,  $M(\omega) \rightarrow 0$

$$\text{Cut-off: } \omega = \frac{1}{CR}$$

COMPLEX POWER:  $\text{Complex} = \text{Real } P + \text{reactive } Q$

\*: indicates complex conjugate

$$I = a + bj$$

$$\Rightarrow I^* = a - bj$$

$$\text{Given: } V = V_m e^{\phi_v j}; I = I_m e^{\phi_I j}$$

$$\Rightarrow S = \frac{V_m e^{\phi_v j} \cdot I_m e^{-\phi_I j}}{2} = \frac{V_m I_m}{2} e^{(\phi_v - \phi_I)j}$$

$$S = S_m \cos(\phi_S) + S_m \sin(\phi_S)j = \frac{V_m I_m}{2} \cos(\phi_v - \phi_I)$$

$$+ \frac{V_m I_m}{2} \sin(\phi_v - \phi_I)j$$

Real Average Power:

$$P_{av} = \text{Re}[S] = \frac{V_m I_m}{2} \cos(\phi_v - \phi_I)$$

Reactive power:

$$Q = \text{Im}[S] = \frac{V_m I_m}{2} \sin(\phi_v - \phi_I)$$

Apparent power:

$$S = \sqrt{P_{av}^2 + Q^2} = \frac{V_m I_m}{2}$$

Power factor:

$$pf = \frac{P_{av}}{S} = \cos(\phi_v - \phi_i)$$

TRANSFER FUNCTION:

$$H = \frac{\text{output}}{\text{input}}$$


$$\text{Voltage gain: } H = \frac{V_{out}}{V_{in}}$$

$$\text{Transfer impedance: } H_Z = \frac{V_{out}}{I_{in}}$$

$$\text{Current gain: } H_Z = \frac{I_{out}}{I_{in}}$$

$$\text{Transfer Admittance: } H_Y = \frac{I_{out}}{V_{in}}$$

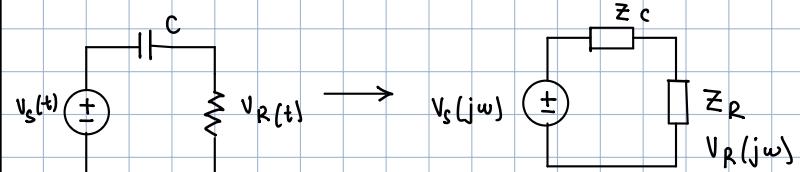
HIGH PASS FILTER: Signals with low  $\omega$  filtered out



$$V_R(j\omega) = \frac{Z_R}{Z_R + Z_C} \cdot V_s(j\omega) = \frac{R}{R + 1/j\omega C} \cdot V_s(j\omega)$$

$$H = \frac{V_R(j\omega)}{V_s(j\omega)} = \frac{j\omega CR}{1 + j\omega CR}$$
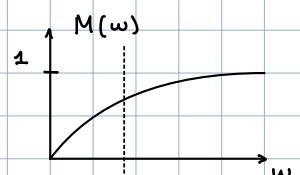
$$M(\omega) = \frac{\omega CR}{\sqrt{1 + (\omega CR)^2}}$$



As  $\omega \rightarrow 0$ ,  $M(\omega) \rightarrow 0$

$\omega \rightarrow \infty$ ,  $M(\omega) \rightarrow 1$

BODE PLOTS: Frequency response plot displayed in logarithmic scale. Horizontal axis: frequency  $\uparrow$   
Unit: decade  $10^N$ . Vertical axis: amplitude or phase unit: dB.  $20 \log_{10}(M(\omega))$

$$H(j\omega) = \frac{\text{output}}{\text{input}} \Rightarrow M(\omega) \angle \phi(\omega)$$

Cut-off frequency:  $P_{\text{out}} < \frac{1}{2} P_{\text{in}}$

$$\frac{V_{\text{out}}}{V_{\text{in}}} < \frac{1}{\sqrt{2}}$$


$$\left| \frac{P_{\text{out}}}{P_{\text{in}}} \right|_{\text{dB}} = 20 \log_{10} \left( \frac{V_{\text{out}}}{V_{\text{in}}} \right)$$

$$20 \log_{10} \left( \frac{1}{\sqrt{2}} \right) = -3 \text{ dB} \Rightarrow \text{filtering begins}$$


Pole: values make denominator = 0  
Zero: values make numerator = 0

$$\frac{1}{1+j\omega R}$$

Table 9-2: Bode straight-line approximations for magnitude and phase.

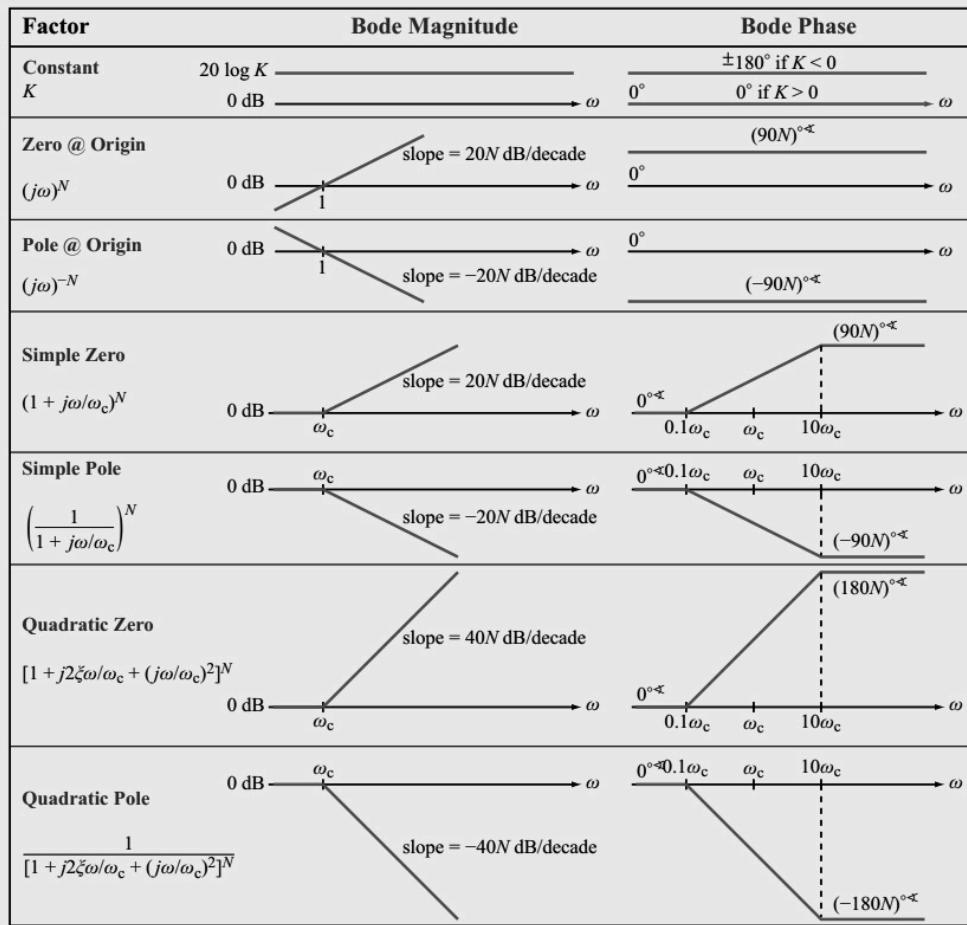

### OPERATIONAL AMPLIFIERS:

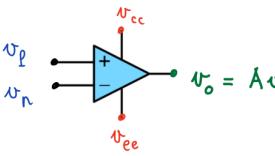


Properties:

- High Gain:  $A = 10^5 - 10^6$
- Differential input:  $v_{\text{in}} = v_p - v_n$
- Linear operating range:
- Saturated by  $+v_{cc}$  and  $-v_{ee}$
- Usually  $v_{ee} = -v_{cc}$

$$\text{Output} = \text{Input} \cdot \text{Gain} \\ = (V_p - V_n) \cdot \text{Gain}$$

### Negative feedback

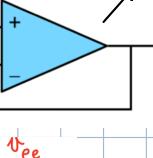

### AMPLIFIER BEHAVIOR MODEL:

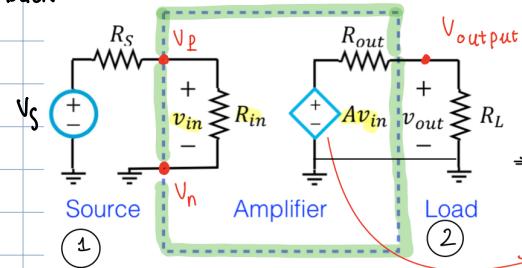



Figure out  $V_{\text{in}}$  first from given  $A$

$$V_{S2} = A \cdot V_{\text{in}}$$

$\Rightarrow$  2 circuits are not connected.

$\rightarrow$  dependent voltage source

### IDEAL MODEL:

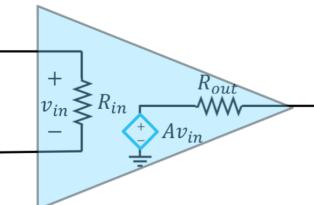

$$V_{\text{in}} = \frac{R_{\text{in}}}{R_{\text{in}} + R_s} V_s$$

$$V_{\text{out}} = V_{S2} \frac{R_L}{R_L + R_{\text{out}}}$$


Assumptions of ideal models:

1.  $i_p = i_n = 0A \Rightarrow$  open circuit

2.  $v_p = v_n$  (voltage is the same, different node).

Table 4-3: Summary of op-amp circuits.

Op-Amp Circuit	Block Diagram
(a)	$v_s \rightarrow G = \frac{R_1 + R_2}{R_2} \rightarrow v_o = Gv_s$
(b)	$v_s \rightarrow G = -\frac{R_f}{R_s} \rightarrow v_o = Gv_s$
(c)	$v_1 \rightarrow G_1 = -R_f/R_1$ $v_2 \rightarrow G_2 = -R_f/R_2$ $v_3 \rightarrow G_3 = -R_f/R_3$ $v_o = G_1v_1 + G_2v_2 + G_3v_3$
(d)	$v_1 \rightarrow G_1 = -\frac{R_2}{R_1}$ $v_2 \rightarrow G_2 = \left(\frac{R_1 + R_2}{R_1}\right)\left(\frac{R_4}{R_3 + R_4}\right)$ $v_o = G_1v_1 + G_2v_2$
(e)	$v_s \rightarrow G = 1 \rightarrow v_o = v_s$
(f)	$v_1 \rightarrow G_1 = \left(\frac{R_1 + R_2}{R_2}\right)\left(\frac{R_{s_2}}{R_{s_1} + R_{s_2}}\right)$ $v_2 \rightarrow G_2 = \left(\frac{R_1 + R_2}{R_2}\right)\left(\frac{R_{s_1}}{R_{s_1} + R_{s_2}}\right)$ $v_o = G_1v_1 + G_2v_2$

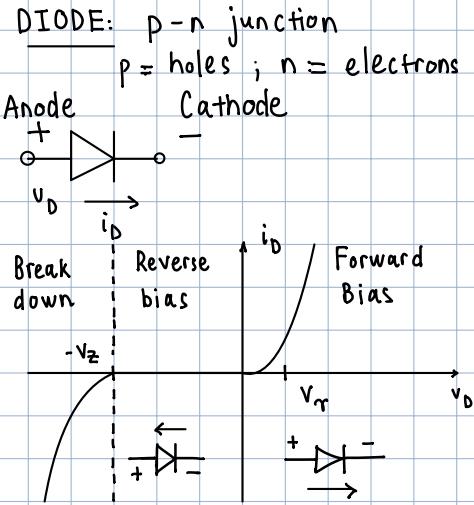Simple Diode Model:


1/ Forward Mode: replaced with 0.7V source if  $i_D > 0$

$i_D > 0 \rightarrow i_D > 0 \rightarrow 0.7V$

2/ Reverse Mode: replaced with open circuit if  $-v_{BRK} < v_D < 0.7$

$v_D < 0 \rightarrow i_D = 0 \rightarrow \text{open circuit}$

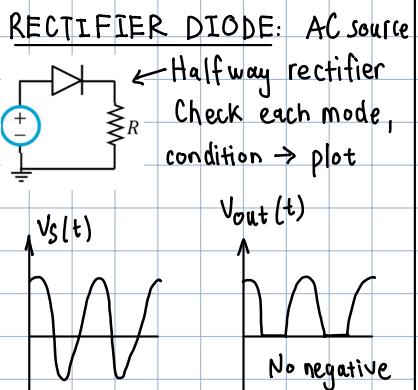Solving problems: Assume all diodes in Reverse mode first. Check conditions. Change accordingly



Mixed AC/DC signal:  
 $v_A(t)$  Output:  
 $v_{AC}(t)$  DC is vertical shift, same frequency.  
 $v_{DC}$

Zener Diode:

3 main states:



- For  $v_D \geq v_{ON}$ : conventional forward-biased diode.  $\Rightarrow$
- For  $v_Z < v_D < v_{ON}$ : open circuit.  $\downarrow v_D < 0.7V$
- For  $v_D \leq v_Z$ : Zener breakdown, voltage across diode is  $-v_Z$ .

Breakdown Mode:


$$v_Z = v_{BRK} + i \cdot r_Z$$

Given like this:

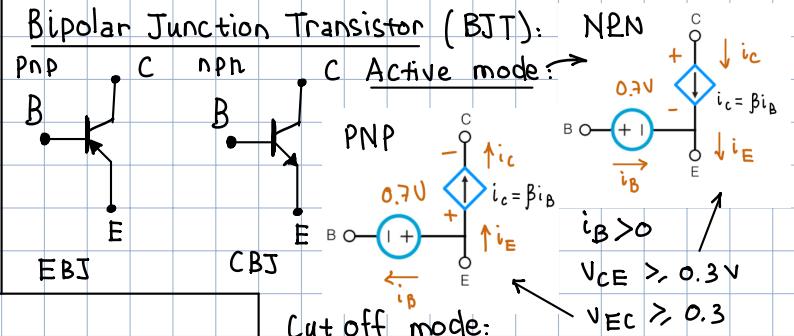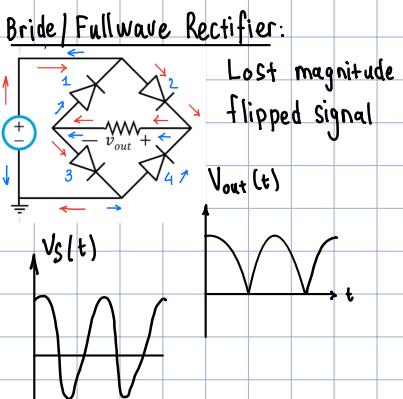
$$\begin{cases} v_Z = 5V @ 1mA \\ r_Z = 25\Omega \end{cases}$$



Cut off mode:

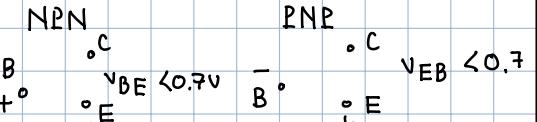

Saturation mode:

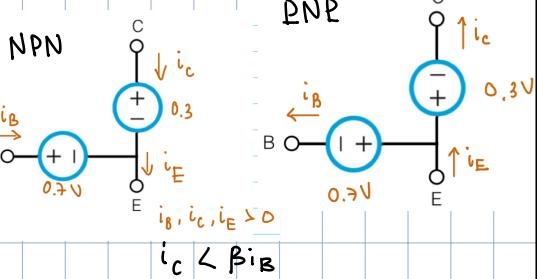

Cut-off  $\rightarrow$  Active  $\rightarrow$  Saturation