
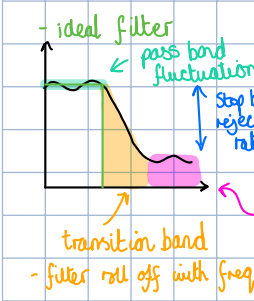


Amplitude of trans. func.
 $|H(j\omega)| = \left| \frac{1}{1+j\omega RC} \right| = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_c})^2}}$

When $\omega = \omega_c$ or $f = f_c$
 $|H(j\omega)| = \frac{1}{\sqrt{2}}$
 \rightarrow Half power 3dB bandwidth

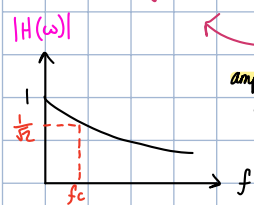periodic: sine waves added equal spaced in frequency
 - lowest freq = freq. of signal
 - all other integer multiples of lower freq. \rightarrow Harmonics





Resistors respond equally to all frequencies
 $V(f) = A \times I(f)$
 Wave forms of V-I associated with resistor vary only in amplitude

Charge accumulates on plates as current passed into it

Capacitance: $q(t) = \int_{-\infty}^t i(t) dt$
 $v(t) = \frac{q(t)}{C} \rightarrow v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$

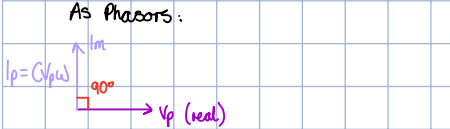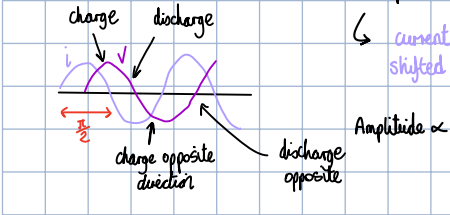For sine waveform
 $v(t) = V_p \sin(\omega t)$
 $i(t) = C V_p \frac{d[\sin(\omega t)]}{dt} = C V_p \omega \cos(\omega t)$
 $i = C V_p \omega \sin(\omega t + \frac{\pi}{2})$
 Amplitude $\propto \omega$ and C



As Phasors:
 $\vec{V}_p = V_p \angle 0$ or $V_p + j0$
 $\vec{I}_p = C V_p \omega \angle \frac{\pi}{2}$ or $0 + j C V_p \omega$

Transfer Function
 $H(j\omega) = |H(j\omega)| \angle \phi(j\omega)$
 Freq. response of RC circuit
 - Also get CL and LF circuits

Frequency response - usable frequency range
 Filters continued...
 Producing Filter
 Frequency dependent impedance

Capacitors
 Stores energy in electric field (Farad)
 Charge accumulates on plates as current passed into it

Inductor
 Stores energy in magnetic field
 induced magnetic field proportional to current flow

Inductive reactance
 $X_L = j 2\pi f L$
 purely imaginary positive increases with freq.

Capacitive Reactance
 - for capacitor, impedance is purely imaginary: reactance negative and decreases with frequency
 $X_C = \frac{1}{j} = \frac{V_p}{j V_p \omega} = -j \frac{1}{2\pi f C}$
 capacitive reactance


Steeper transition bands

As Phasors:
 $\vec{V}_p = V_p \angle 0$ or $V_p + j0$
 $\vec{I}_p = C V_p \omega \angle \frac{\pi}{2}$ or $0 + j C V_p \omega$

Analogue


Bandwidth
 frequency domain \rightarrow frequency spectrum
 Amplitude-phase graph
 difference between half power frequencies
 $-3dB$ or $V = \frac{V_{max}}{\sqrt{2}}$

Transfer function continued... (top right)
 $|H(\omega)|$ in dB
 $= 20 \log_{10} \frac{1}{\sqrt{1+(\frac{\omega}{\omega_c})^2}}$
 $\omega < \omega_c$ $|H(\omega)| = 1$ or 0dB
 $\omega = \omega_c = \frac{1}{\sqrt{2}}$ = -3dB
 $\omega \gg \omega_c = -20 \log \frac{\omega}{\omega_c}$
 high freq amplitude decreases at rate of 20dB for f up of 10x (20dB per decade roll off)

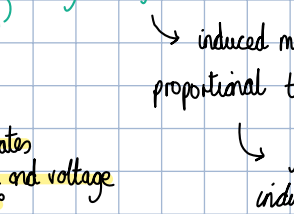

for sine waveform inductor results in similar but opposite equations.
 $v(t) = L \frac{di(t)}{dt}$

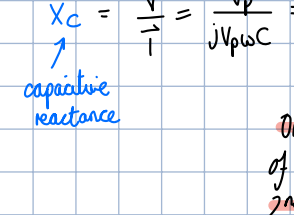Output impedance of 1st and input of 2nd change respective freq. response \rightarrow use buffers between \rightarrow elim. loading effect



Cascading Filters
 - Can create band-pass and band-stop filters
 e.g. band-pass
 high + low pass cascaded

