
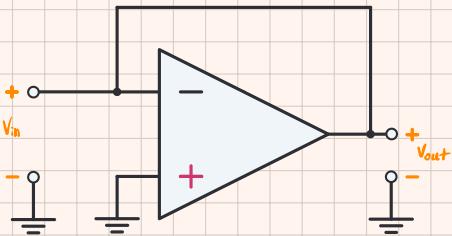


## Voltage Follower (Buffer)

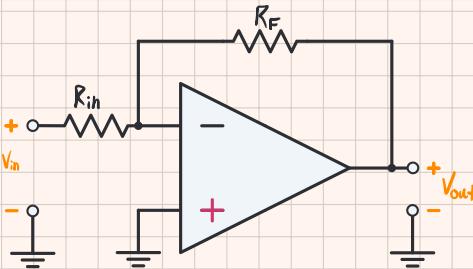


$$A_v = \frac{V_{out}}{V_{in}} = 1$$

## Inverting Amplifier




$$A_v = \frac{V_{out}}{V_{in}} = -\frac{R_F}{R_{in}}$$

## Differential Amplifier

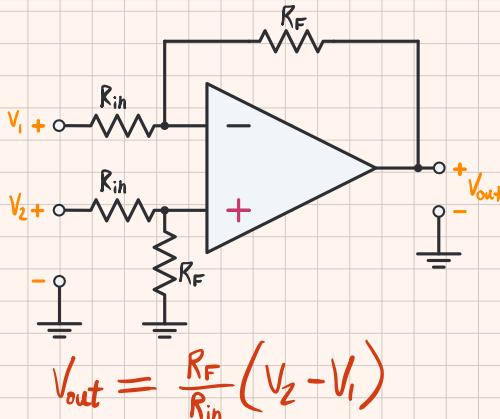


$$V_{out} = \frac{R_F}{R_{in}}(V_2 - V_1)$$

## Non-Inverting Amplifier

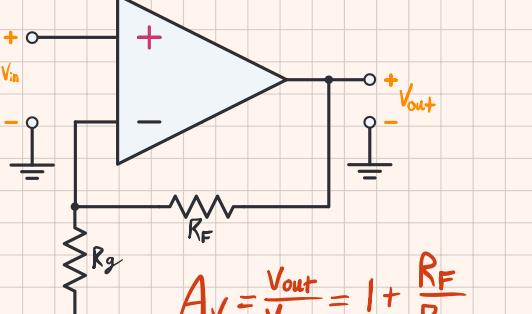


$$A_v = \frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_g}$$

## Inverting Integrator

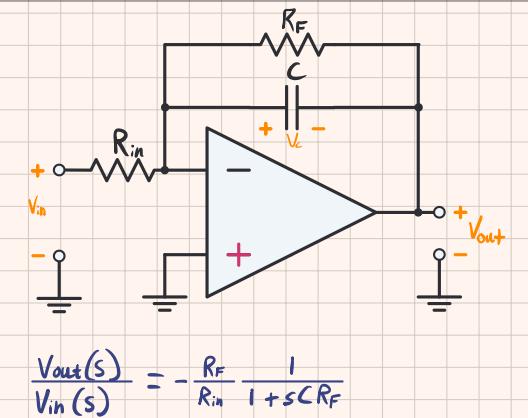


$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_F}{R_{in}} \frac{1}{1+sCR_F}$$

## Summing Amplifier

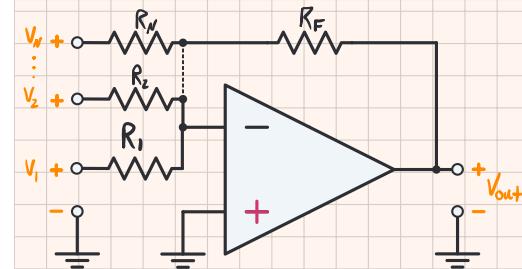

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_N}{R_N} \right)$$

## Inverting Differentiator

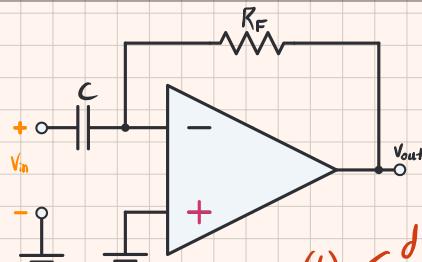

$$i(t) = C \frac{d}{dt} V_{in}(t)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = -sCR \quad V_{in}(t) = -CR \frac{d}{dt} V_{in}(t)$$

# Common Op-Amp Configurations