

Sine r.m.s

$$V(t) = V_{oc} + V_0 \sin(\omega t + \phi)$$

$$V_{rms} = \frac{V_0 - pk}{\sqrt{2}}$$

$$I_{rms} = \frac{I_0 - pk}{\sqrt{2}}$$

for sine waveform through origin $V_{oc} = 0$

$$V(t) = V_0 \sin(\omega t + \phi) = \frac{1}{T} \int_0^T \sin(\omega t + \phi) dt$$

Slew Rate

for non-periodic waveform:
 period/frequency doesn't apply
 → slew rate can still be defined
 → not found mathematically, only by observing signal for long time.

$\max \left(\left| \frac{dv}{dt} \right| \right)$

→ gradient of V-t waveform

square wave $\approx \infty$

r.m.s value:
 equivalent amplitude of D.C. only signal for which resistor dissipate same power

sine passing through diode



Phasors
 - rotating vectors

Magnitudes are V_2 and V_1 length

ϕ , angle between is phase difference

V_2 is leading
 V_1 is lagging

$\phi = \frac{1}{T} \times 2\pi$

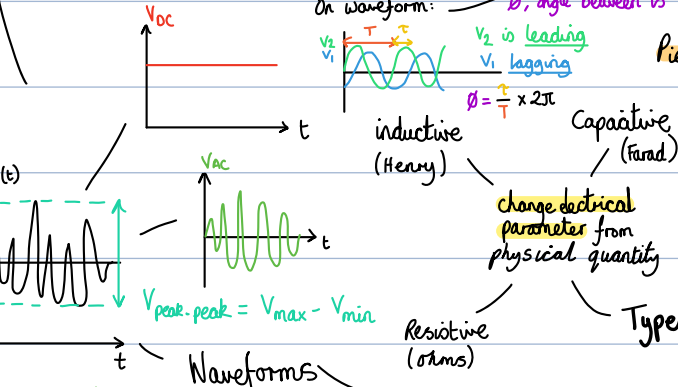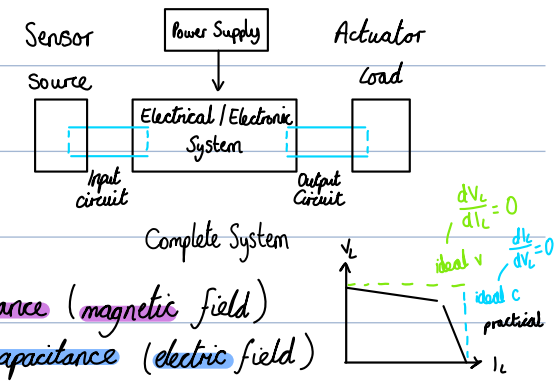


Features

Never perfect reflection of associated quantities
 → noise, interference and distortion

Small signals
 → insufficient power drive actuators

Mean value (\bar{v})
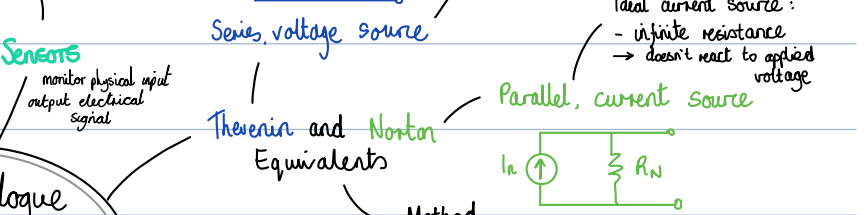
$$= \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} v(t) dt$$


Processing

Amplification

Storage

Interpretation

Display

Actuation

$V_o = A_v (V_+ - V_-)$

Sensors
 monitor physical input output electrical signal

Types

Resistive (ohms)

Piezoelectric (strain)

Photoelectric (light)

Inductance (magnetic field)

Capacitance (electric field)

Types

Resistive (ohms)

Piezoelectric (strain)

Photoelectric (light)

Inductance (magnetic field)

Capacitance (electric field)

Filtering

described by transfer function

$$H(f) = \frac{V_{out}(f)}{V_{in}(f)}$$

in freq. domain

or $|H(f)| (dB) = 20 \log_{10} \left(\left| \frac{V_{out}(f)}{V_{in}(f)} \right| \right)$

dB scaled gives straight line approximations

Op-Amps


- ideal voltage amplifiers

- differential input, single-ended output

$R_o = 0$
 → V_o unaffected by load value

$R_i \approx \infty$
 → draws no current from source
 → $I_i = 0$
 → $V_i = 0$

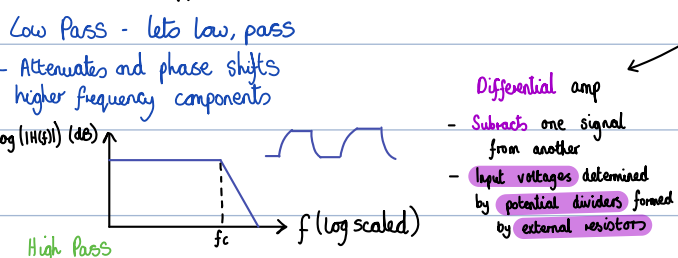$V_{gain} (A_v) \approx \infty$
 → voltage ranges limited by PSU clipping



Unity Gain Buffer
 (aka voltage follower / V buffer)

- Non-inverting

- Gain = 1

→ buffer

- Extreme of non-inverting where $R_2 = 0, R_1 = \infty$

Non-Inverting amp

$V_o = V_+ = V_i$

→ determined by R_i and potential divider formed by R_1 and R_2


$V_o = V_i = V_o \frac{R_1 + R_2}{R_1}$

$G_v = \frac{V_o}{V_i} \rightarrow G_v = 1 + \frac{R_2}{R_1}$

- Currents I_1 and I_2 equal and opposite

→ $\frac{V_o}{R_2} = -\frac{V_i}{R_1}$

∴ $G_v = -\frac{R_2}{R_1}$

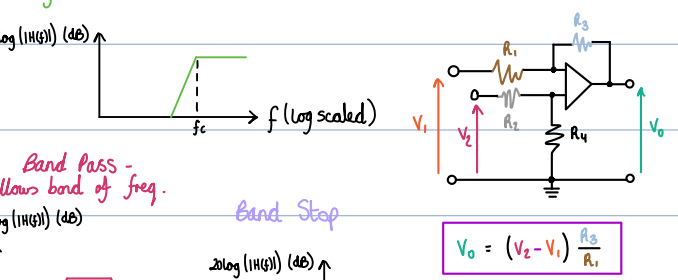

Cascading Amps

- Amps in series:

$A = A_1 \times A_2 \times A_3$

$A (dB) = A_1 (dB) + A_2 (dB) \dots$

increases amp.

Clipping: limits max range of signal

→ e.g. sine clipped → square

